

## Week 6 Questions and Answer Key

- Day 1, Presidents Day
- Day 2, Integrals Test
- Day 3, questions 1-4
- Day 4, questions 5-9
- Day 5, questions 10-14

1. The current in a circuit was  $i = 4t^3$  amps. How many coulombs were transmitted in 3 seconds?

$$q = 81 \text{ coulombs}$$

2. A  $80\mu f$  capacitor is charged to 100 volts. We then apply a current  $i_c = 0.04t^3$  amps in the same polarity as the initial charge. After how many seconds will the capacitor voltage reach 225 volts?

$$t = 1 \text{ second}$$

3. The voltage applied to a circuit was  $v = 2t + 1$  volts. If the current followed the equation  $i = 0.03t$  amperes, find the energy  $w$  delivered from  $t = 0$  to  $t = 50$  seconds.

$$w = 2.5375K \text{ watts}$$

4. A 110 turn winding carries a flux of 0.8 webers. If we now want to vary the flux so that a voltage  $v_{ind} = -5t^2$  volts appears in the winding, what equation must the flux through the winding follow?

$$\phi = \frac{t^3}{66} + 0.8 \text{ webers}$$

5. A DC current of 0.3 ampere flows in a 15 henry inductor. Superimposed on this DC is a varying current such that the voltage  $v_{ind} = 120t^{\frac{1}{3}}$  volts appears in the inductor. Find the instantaneous total current when  $t = 1$  second (assume that the DC and AC currents have the same polarity when  $t = 1$  second).

$$i = 6.3 \text{ or } -6.3 \text{ amps}$$

6. An inductance of 8 henrys is connected in parallel with a  $12\Omega$  resistor. Apply to this circuit a voltage  $v = 20t^2$  volts. If  $i = 0$  when  $t = 0$ , find an equation for  $i$ .

$$ig = \frac{5t^2}{3} - \frac{5t^3}{6} \text{ amps}$$

7. If we apply a voltage  $v = 90t^{\frac{1}{2}}$  to a circuit consisting of a 30 henry inductance shunted by a  $50\Omega$  resistance, what current flows when  $t = 4$  seconds? (let  $i = 0$  when  $t = 0$ ).

$$ig = -12.4 \text{ amps}$$

8. If we apply a voltage  $v = 20t^4$  volts across a parallel  $RL$  combination, where  $R = 500\Omega$  and  $L = 40$  henrys, find the total current when  $t = 0.2$  seconds. Let  $i = 4\mu\text{A}$  when  $t = 0$ .

$$ig = 36\mu\text{A}$$

9. In a parallel  $RL$  circuit,  $R = 5\Omega$  and  $L = 0.2$  henrys. If a voltage  $v = t^{\frac{3}{2}} + 2$  volts were applied, what would the current  $i$  be when  $t = 4$  seconds? Assume  $i = 0.4$  amps when  $t = 0$ .

$$ig = 101.6 \text{ amps}$$

10. A current  $i = 0.005t^{\frac{1}{2}}$  amps flows in a parallel  $RC$  circuit where  $R = 8.8 \times 10^4\Omega$  and  $C = 1\mu\text{f}$ . Find a formula for the voltage across the circuit as a function of time  $t$ . Assume the capacitor to be initially discharged.

$$vg = 440t^{\frac{1}{2}} + 3.333 \times 10^3 t^{\frac{3}{2}} \text{ volts}$$

11. The current function  $i = 1 \times 10^{-3}t^{\frac{1}{2}}$  amperes is applied to a series  $RC$  circuit where  $R = 8.8 \times 10^4\Omega$  and  $C = 1\mu\text{f}$ . Find a formula for the impressed voltage as a function of time  $t$ . (Assume the initial capacitor charge to be 100v.)

$$vg = 88t^{\frac{1}{2}} + 666.667t^{\frac{3}{2}} + 100 \text{ volts}$$

- 
12. A series  $LC$  circuit where  $L = 0.1$  henry and  $C = 100\mu f$  has applied to it a current  $i = 0.1A$  from  $t = 0$  onward. Find (a) the formula for the voltage across the circuit, and (b) the rate of change at  $t = 2$  sec. (assume  $v_c = 0$  when  $t = 0$ )

a.  $vg = 1000t$

b.  $\frac{dv}{dt} = 1000v/s$

13. A series circuit has these constants:  $R = 5K\Omega$ ,  $L = 200$  henrys, and  $C = 20\mu f$ . If we supply to the circuit a current  $i = 0.02t^2$  amperes, at what rate does the voltage across the circuit change when  $t = 0.2$  seconds?

$\frac{dv}{dt} = 72v/s$

14. In a series  $RCL$  circuit, let  $R = 10\Omega$ ,  $C = 10,000\mu f$ , and  $L = 10$  henrys. Through this circuit we pass a current  $i = 1 - t^2$  amps. Find the total voltage  $v$  across this circuit when  $t = 4$  seconds. Assume  $v = 0.25$  volts when  $t = 1$  second.

a.  $vg = -178v$